



ELECTROVERT 2018

The Performers' creed




Name of the Event: **Circuit-Tech (Expert)**
Candidate's Code:

Date: **08 Sept 2018**
Time: **40 min**

Instructions

- All **questions** are compulsory.
- All questions are compulsory and carries equal amount of marks.
- Use of calculators is allowed.
- Use of mobile is strictly prohibited

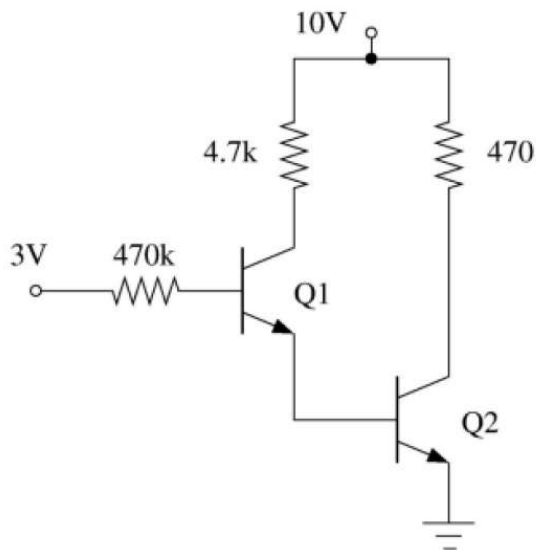
Q1 .Find i_{C2} (Si BJTs with $\beta_1=100$ and $\beta_2=50$).




Q 2. Obtain the triangular wave at output if you are provided with sine wave as input, two op amps ,fixed voltage source, suitable resistors and capacitors, +Vcc , -Vcc? Draw circuit diagram for your solution ?

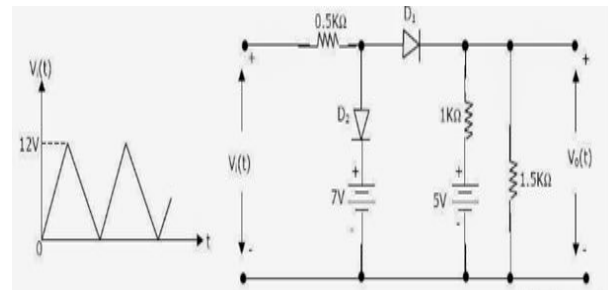Q3. A triangular voltage waveform $V_i(t)$ is applied at the input to the circuit shown. Assume the diodes to be ideal.

- Determine the output $V_o(t)$
- Nearly sketch the output waveform superimposed on the input $V_i(t)$ and label the key points.



Q4.

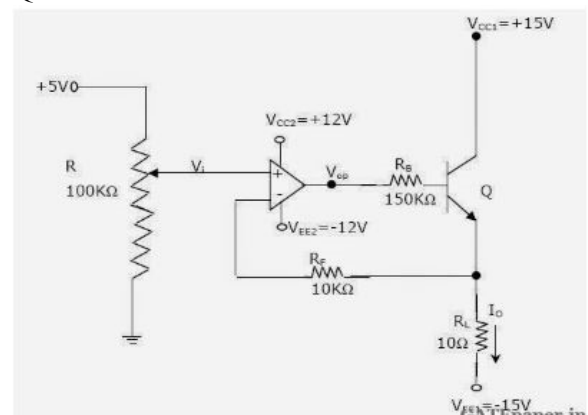

- In which mode is the BJT operating (cut off /active/saturation) ?Justify your answer.
- Obtain an expression relating the output current I_o and the input voltage V_i .
- Determine I_o and V_o if $V_i=2$ Volts. Assume $\beta=99$, $V_{BE}=0.7$ V