



ELECTROVERT 2018

The Performers' creed



Name of the Event: Proignito
Candidate's Code:

Date: 8 SEPT, 2018
Time: 30 min

Instructions

- Use of mobile is not allowed.
- Use of scientific calculator is allowed.
- Every questions carry one mark with no negative marking.

1. What is the logic which controls a staircase light associated with two switches A and B located at the bottom and top of the staircase respectively?

- A. OR
- B. AND
- C. X-OR
- D. X-NOR

2. What are the values of R1 and R2 respectively in the expression

$$(235)R_1 = (565)_{10} - (1065)R_2 ?$$

- A. 8,16
- B. 16,8
- C. 6,16
- D. 12,8

3. In 1-to 32 demultiplexer, how many select lines are required?

- A. 2
- B. 3
- C. 4
- D. 5

4. Which of the following is NOT available in terminal mode?

- A. POWER
- B. GROUND
- C. INVERT
- D. BIDIR

5. A latch is _____ sensitive

- A. both level and edge
- B. edge
- C. level
- D. None

6. The fast logic family is

- A. ECL
- B. DRL
- C. TRL
- D. TTL


A. Weighted code

B. Self complementing code

C. Non weighted code


D. Alphanumeric code

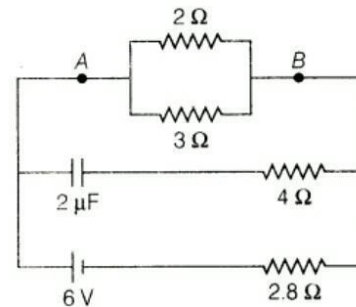8. Calculate the steady current through the 2 ohm resistor in the circuit shown below.



- A. 0.75 A
- B. 0.6 A
- C. 1.5 A
- D. 0.9 A

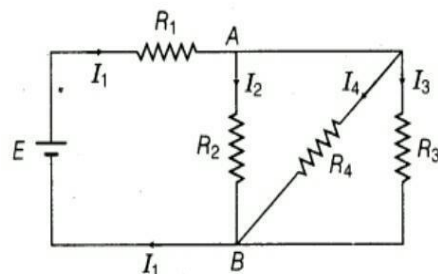9. In the circuit shown, $R_1=4\text{ ohm}$, $R_2=R_3=15\text{ ohm}$, $R_4=30\text{ ohm}$ and $E=10\text{ V}$. What is the equivalent resistance of the circuit and also determine the relation between I_1 , I_2 and I_3, I_4 .



- A. 10 ohm, $I_1=(3/2) \times I_2$, $I_3=(1/2) \times I_4$
- B. 5 ohm, $I_1=(1/2) \times I_2$, $I_3=(3/2) \times I_4$
- C. 10 ohm, $I_1=(5/2) \times I_2$, $I_4=(1/2) \times I_3$
- D. 5 ohm, $I_1=(2/3) \times I_2$, $I_4=(3/2) \times I_3$

10. A battery of 10 V and negligible internal resistance is connected across the diagonally opposite corners of a cubical network consisting


of 12 resistors each of 1 ohm resistance.
Determine the equivalent resistance and the total current in the network.

- A. $R=1/6$ ohm, $I= 1$ A
- B. $R=6/5$ ohm, $I=1.5$ A
- C. $R=2/3$ ohm, $I= 1$ A
- D. $R=5/6$ ohm, $I=2$ A

11. The simplified form of the Boolean expression $(X + Y + XY)(X + Z)$ is


- A. $X + Y + Z$
- B. $XY + YZ$
- C. $X + YZ$
- D. $XZ + Y$
- E. None of the above

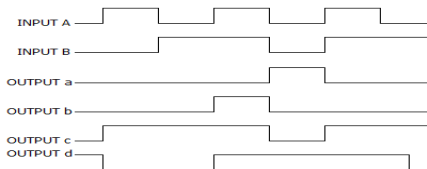12. For a two-input XNOR gate, with the input waveforms as shown below, which output waveform is correct?



- A. a
- B. b
- C. c
- D. d

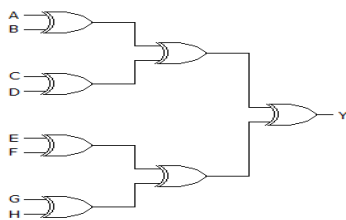13. The 8-input XOR circuit shown has an output of $Y = 1$. Which input combination below (ordered A – H) is correct?



- A. 10111000
- B. 11100111
- C. 10111100
- D. 00111011

14. 2's complement representation of a 16 bit number (one sign bit and 15 magnitude bit) is FFFF. Its magnitude in decimal representation is

- A. 0
- B. 1
- C. 32676

D. 65, 535

15. Mod-6 and mod-12 counters are most commonly used in:

- A. frequency counters
- B. multiplexed displays
- C. digital clocks
- D. Power consumption meters

16. The signal voltage gain of an amplifier, A_v , is defined as:

- A. $A_v = V_{in}/V_{out}$
- B. $A_v = I_C \times R_C$
- C. $A_v = R_C/R_E$
- D. $A_v = R_C/R_L$

17. $I_c = \frac{\alpha}{1-\alpha} I_B + \dots$

- A. I_{CBO}
- B. I_{CEO}
- C. I_C
- D. $(1-\alpha)I_B$

18. The filter circuit results into best voltage regulation

- A. Capacitor input
- B. Resistor input
- C. Choke input
- D. None of these

19. What is the phase difference between input and output voltages of transistor connected in common collector arrangement?

- A. 0°
- B. 90°
- C. 180°
- D. -90°


20. Which of the following IC is not used in AOI logic?

- A. 7408
- B. 7432
- C. 7404
- D. 7402

21. Which of the following is a false relation?


- A. $AB + \bar{A}C = (A+C)(\bar{A}+B)$
- B. $(A+B)' = \bar{A} \cdot \bar{B}$
- C. $AB + \bar{A}C + BC = A\bar{B} + A\bar{C}$
- D. $[(\bar{A} + \bar{A} \cdot \bar{B}) \cdot (\bar{B} + \bar{B} \cdot \bar{C})]' = A + B$

22. Find the equivalent delta circuit.

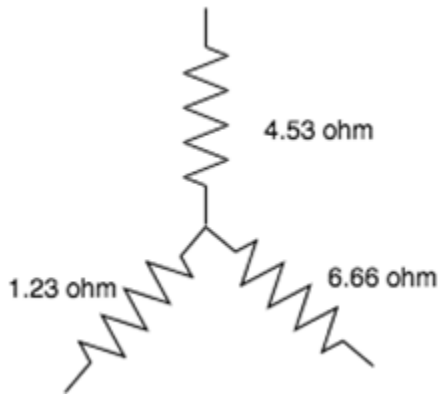

- A. 3ohm, 10ohm, 5ohm
- B. 3ohm, 10ohm, 15ohm
- C. 3ohm, 1ohm, 5ohm
- D. 3ohm, 10ohm, 6ohm

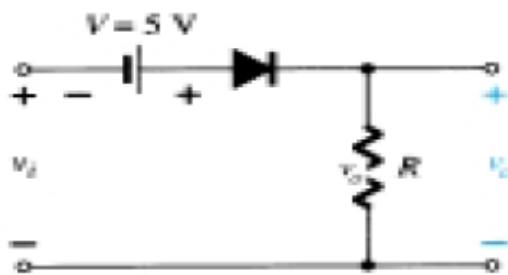23. For a sinusoidal input of $20 V_{\text{peak}}$ to the given circuit, what is the peak value of the output waveform?



- A. 20 V
- B. 25 V
- C. 0 V
- D. -25 V

24. For a BJT, for common base configuration the input characteristics are represented by a plot between which of the following parameters?

- A. V_{BE} and I_E
- B. V_{BE} and I_B
- C. V_{CE} and I_C
- D. None of the mentioned

25. In a bridge full wave rectifier, the input sine wave is $250\sin 100\pi t$. The output ripple frequency of rectifier will be

- A. 50Hz
- B. 200Hz

- C. 100Hz
- D. 25Hz

26. which of the following statement is false for series resonance RLC circuit?

- A. power factor=1
- B. $Z_{\text{min}}=R$
- C. $Q=L/RC$
- D. $F_r = \frac{1}{2\pi(LC)^{1/2}}$


27. which of the following quantity remains constant in transformer ?

- A. power
- B. frequency
- C. both
- D. none of these

28. In the toggle mode a JK flip-flop has

- A. $J=0, K=0$
- B. $J=1, K=1$
- C. $J=0, K=1$
- D. $J=1, K=1$

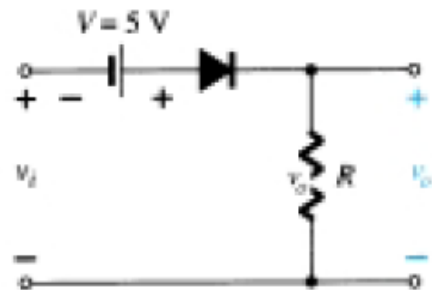29. What is the circuit in the given diagram called?



- A. Clipper
- B. Clamper
- C. Rectifier
- D. None of the mentioned

Answer: a

30. In a Zener diode with high breakdown voltage

- A. Both P and N are heavily doped.
- B. Both P and N are lightly doped.
- C. Either P or N are lightly doped.
- D. None of the above.