



ELECTROVERT 2018

The Performers' creed




Name of the Event: **Circuit-Tech (Novice) Round2**
Candidate's Code:


Date: **09 Sept 2018**
Time: **45 min**

- All **questions** are compulsory.
- All questions are compulsory and carries equal amount of marks.
- Use of calculators is allowed.
- Use of mobile is strictly prohibited.

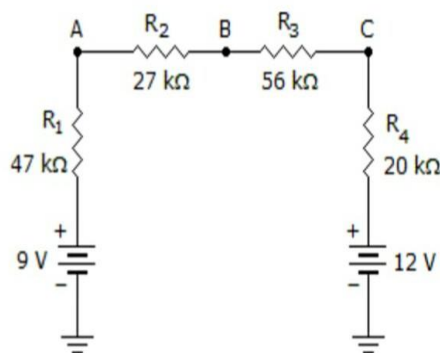
1. How much current flows in the given circuit?



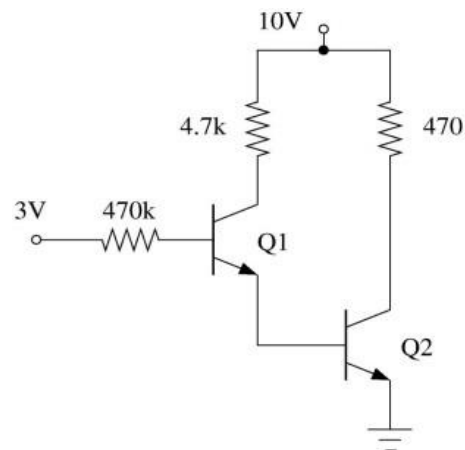3. Find i_{C2} (Si BJT with $\beta_1=100$ and $\beta_2=50$).




2. What is the total resistance?

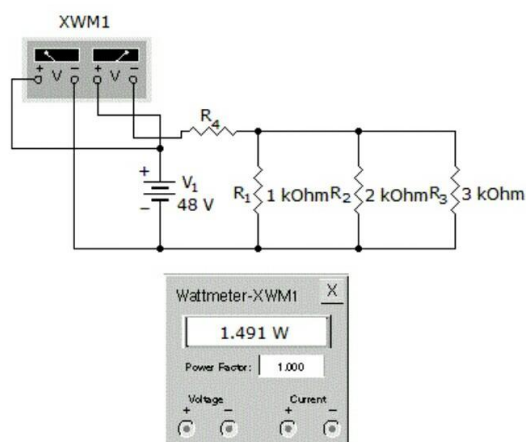

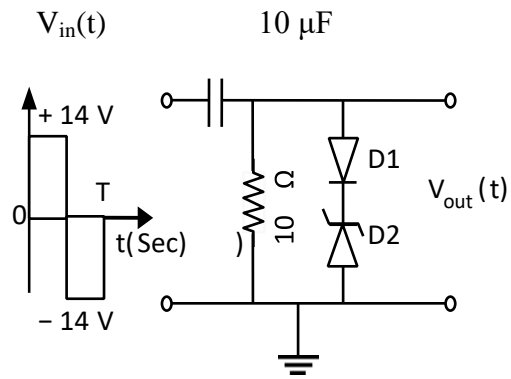4.

In the figure, D1 is a real silicon pn junction diode with a drop of 0.7V under forward bias condition and D2 is a zener diode with breakdown voltage of -6.8V . The input $V_{in}(t)$ is a periodic square wave of period T, whose one period is shown in the figure.



Assuming $10\ \tau \ll T$. Where τ is the time constant of the circuit, the maximum and minimum values of the output waveform are respectively?